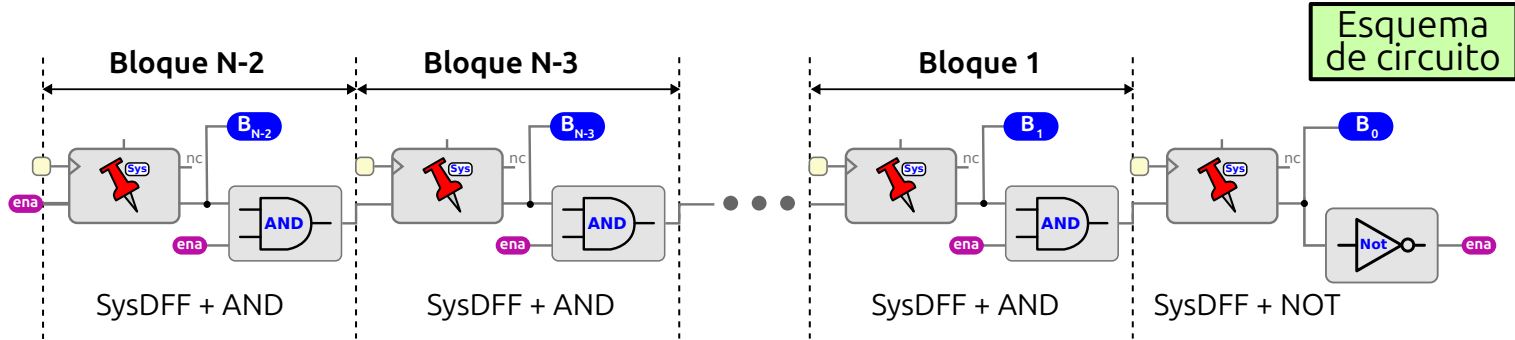


Circuito en Icestudio




Recursos: LC: N+1 IO: N+1

N-1 puertas AND

N-1 Biestables

Cronograma

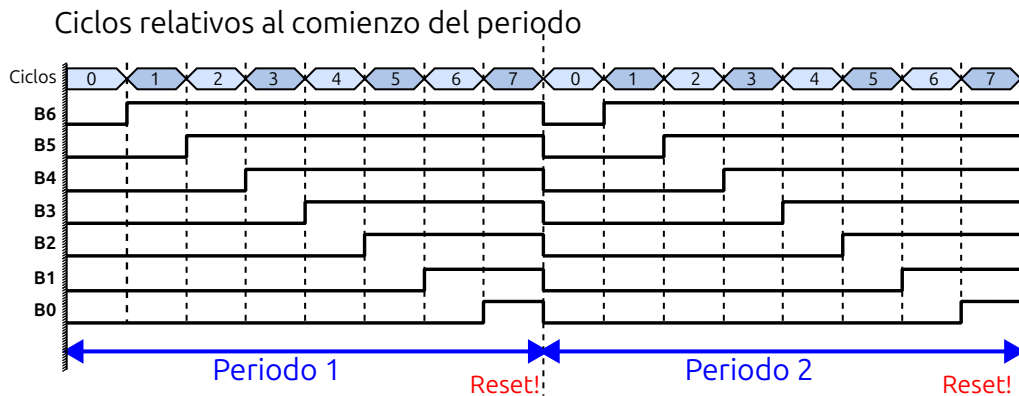



Estado

Ciclo	B _{N-2}	B _{N-3}	...	B ₁	B ₀
0	0	0	...	0	0
1	1	0	...	0	0
2	1	1	...	0	0
...
N-2	1	1	...	1	0
N-1	1	1	...	1	1
					MAX
					Reset!
0	0	0	...	0	0
1	1	0	...	0	0
2	1	1	...	0	0
...
N-2	1	1	...	1	0
N-1	1	1	...	1	1
					MAX
					Reset!

Caso de estudio N=8


N-1 bits de almacenamiento

Diagrama de estado

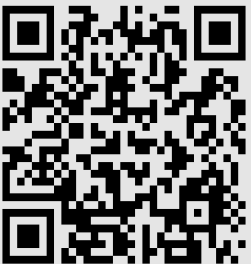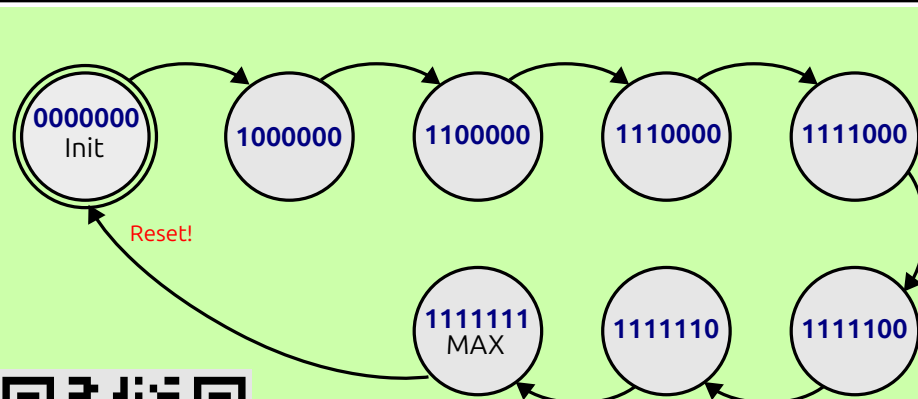

Caso de estudio N=8

Resultado

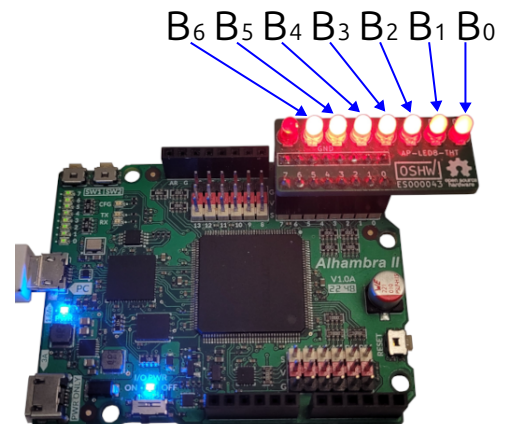

Efecto óptico:
7 LEDs "encendidos"

064

unary-modn

Contador unario módulo N

TUTORIAL (Obijuan)

